

# Amaranth (2, practice)

Hardware System Design


Spring, 2023

# Outline

- **Prevent metastability**
- Practice
  - Implement PE, stacked PE
 
## Flip-Flops – Timing considerations


- ▶ Because of the construction of a flip-flop [1], the input must be held steady in a period around the rising edge of the clock.
- ▶ **Setup time** is the minimum amount of time the data input should be held steady before the clock event, so that the data is reliably sampled by the clock.
- ▶ **Hold time** is the minimum amount of time the data input should be held steady after the clock event, so that the data is reliably sampled by the clock.



[1] <https://www.edn.com/understanding-the-basics-of-setup-and-hold-time/>
 
# Flip-Flops – Metastability


- ▶ If setup and hold time are not respected, flip-flops are subject to a problem called **metastability**
- ▶ The result is that the output may behave unpredictably, taking many times longer than normal to settle to one state or the other, or even oscillating several times before settling.



<https://youtu.be/5PRuPVIjEcs>

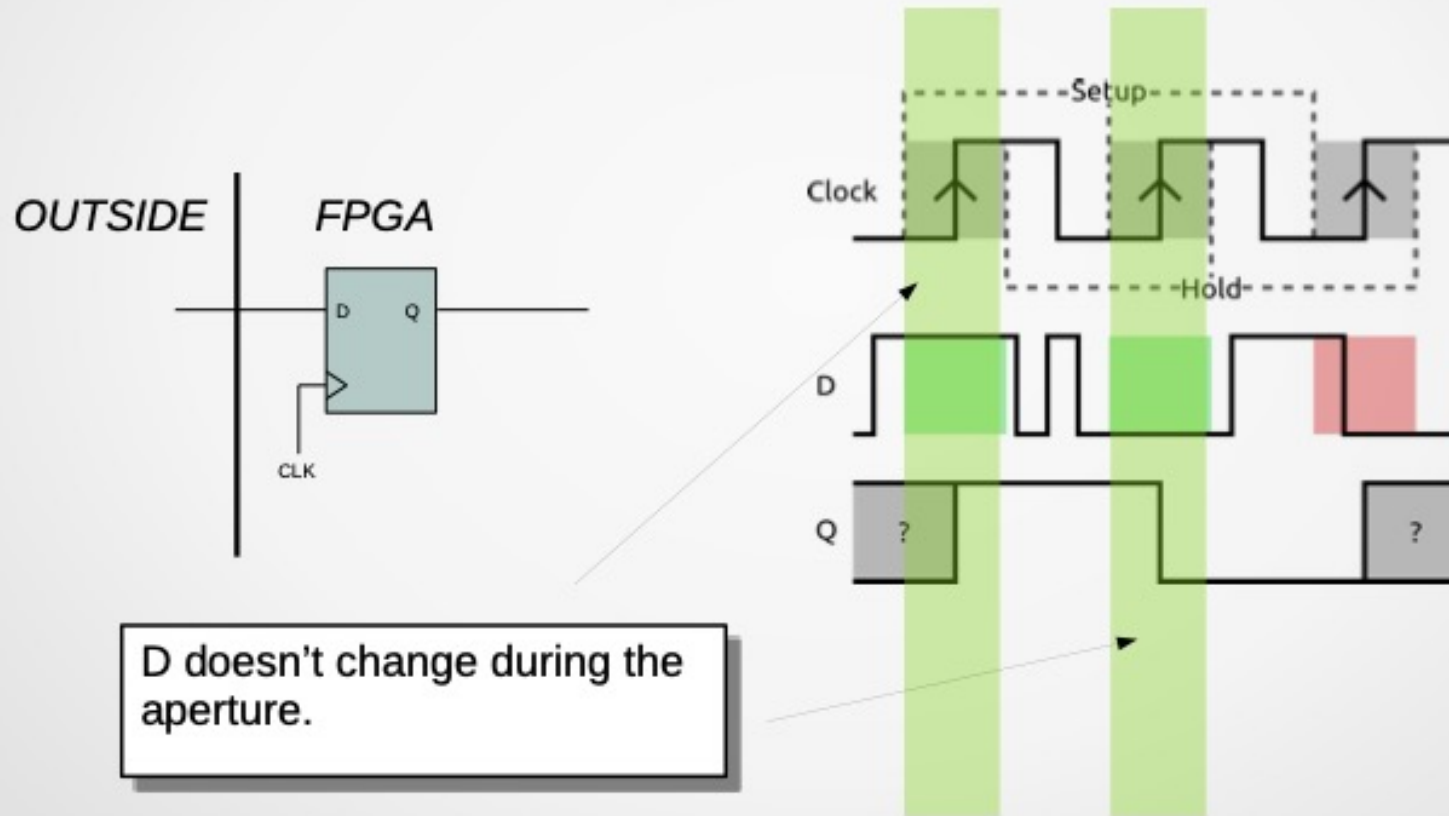
## Three main reasons for metastability problem (1/3)

- ▶ An external signal (user input) is read inside the FPGA:



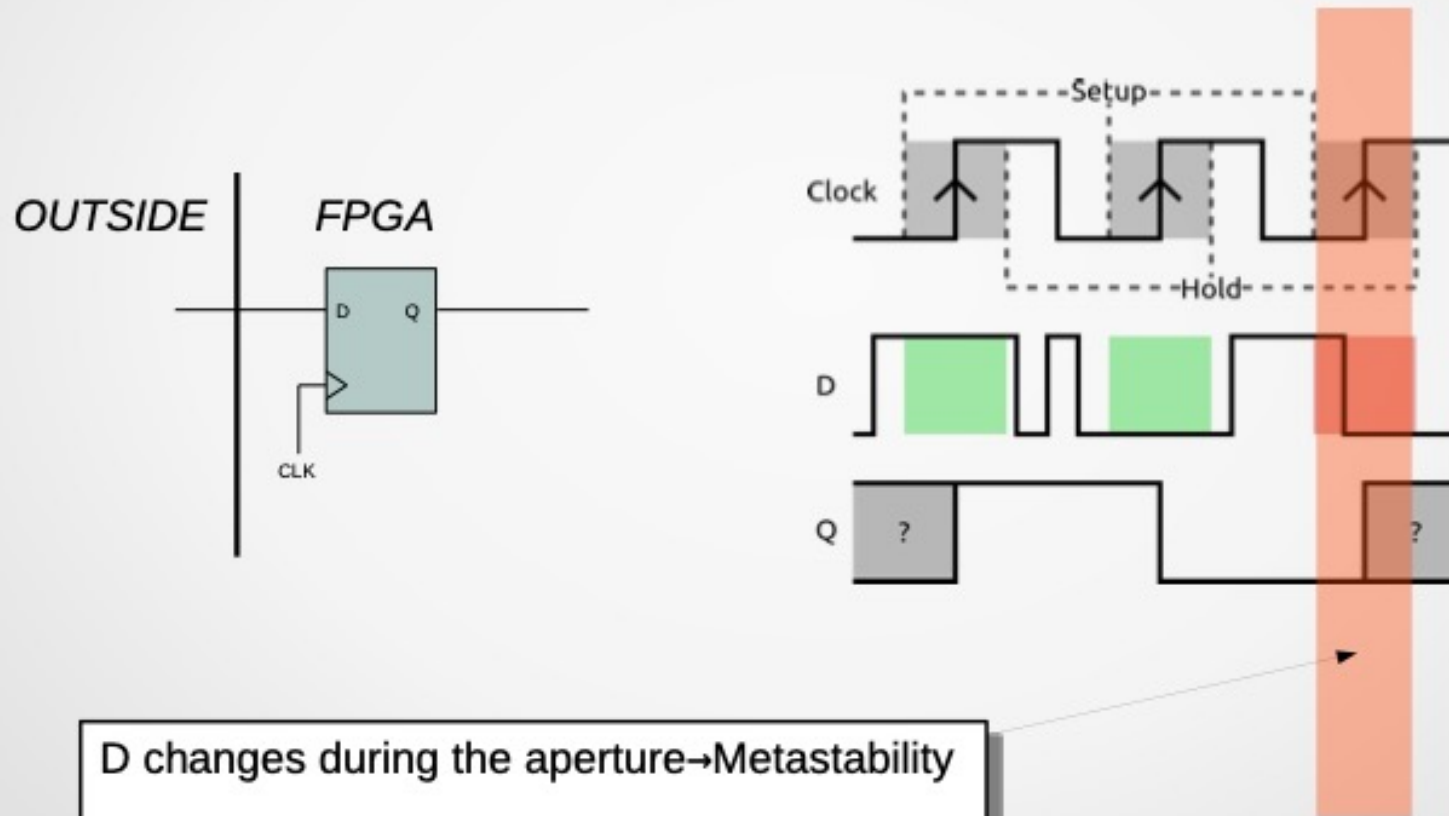
## Three main reasons for metastability problem (1/3)

- ▶ An external signal (user input) is read inside the FPGA:



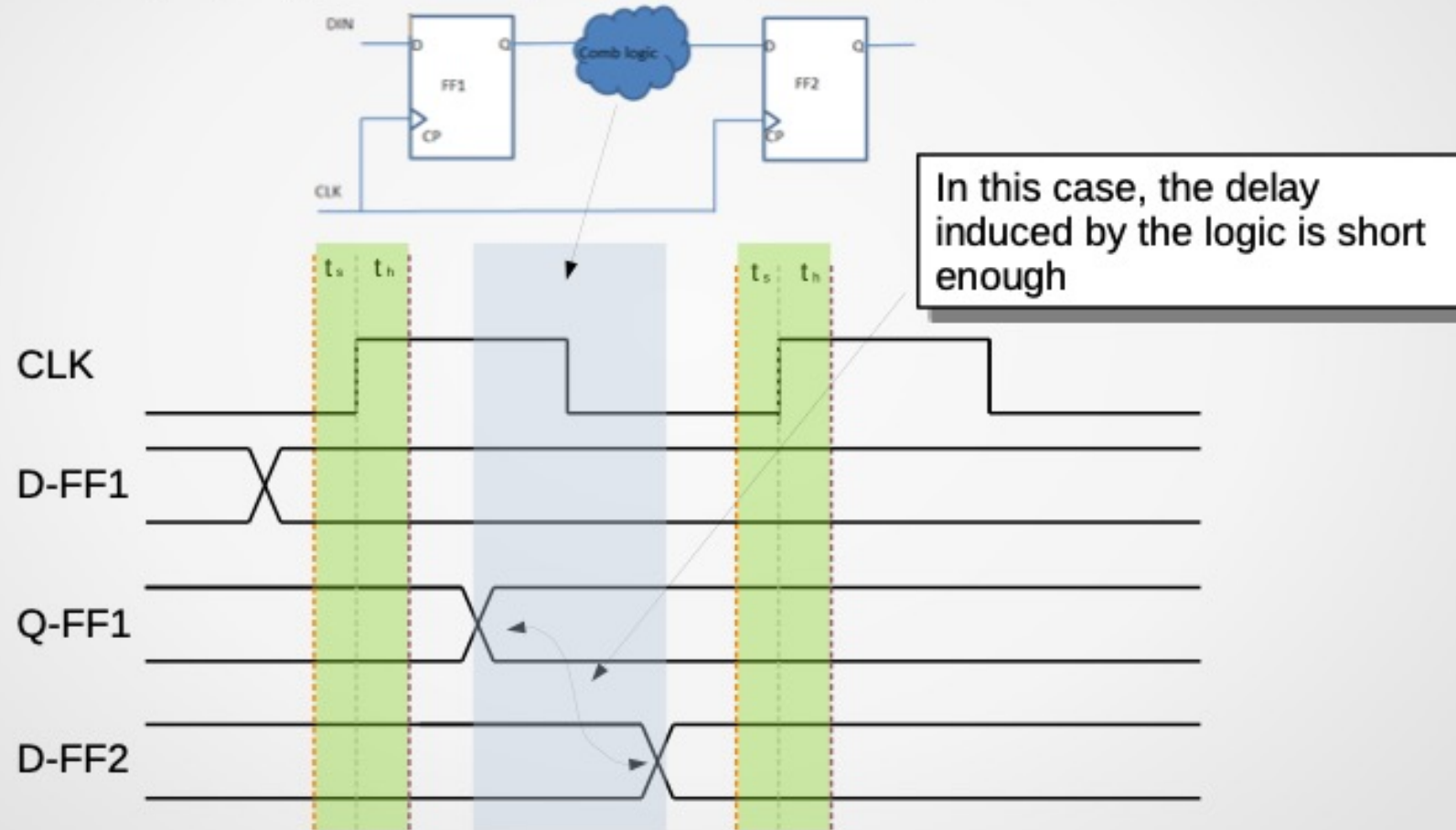
## Three main reasons for metastability problem (2/3)

- ▶ Too much logic (delay) between flip-flops (setup violation):


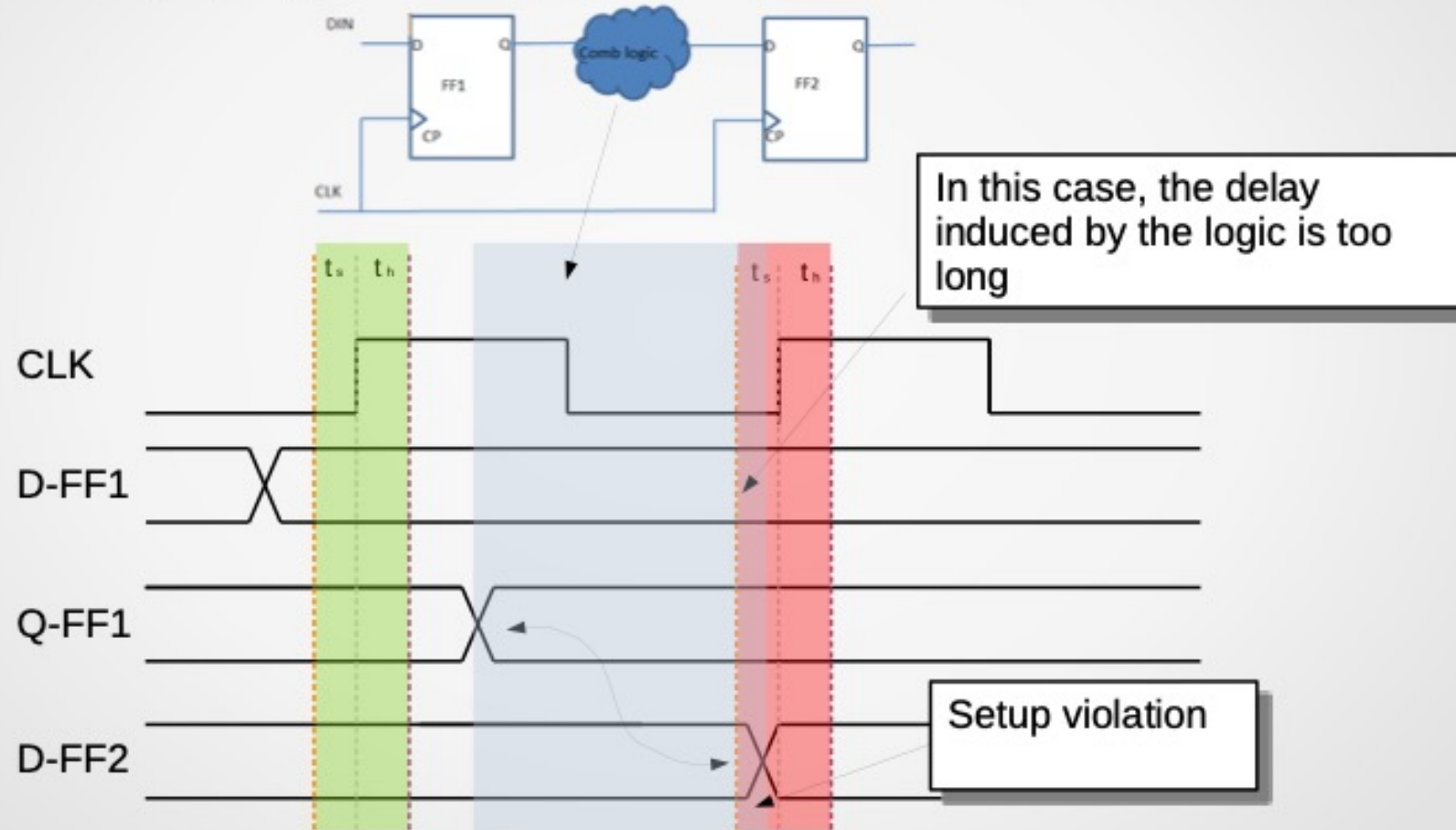
## Three main reasons for metastability problem (2/3)


- ▶ Too much logic (delay) between flip-flops (setup violation):





## Three main reasons for metastability problem (3/3)

### ► Multiple clock domains

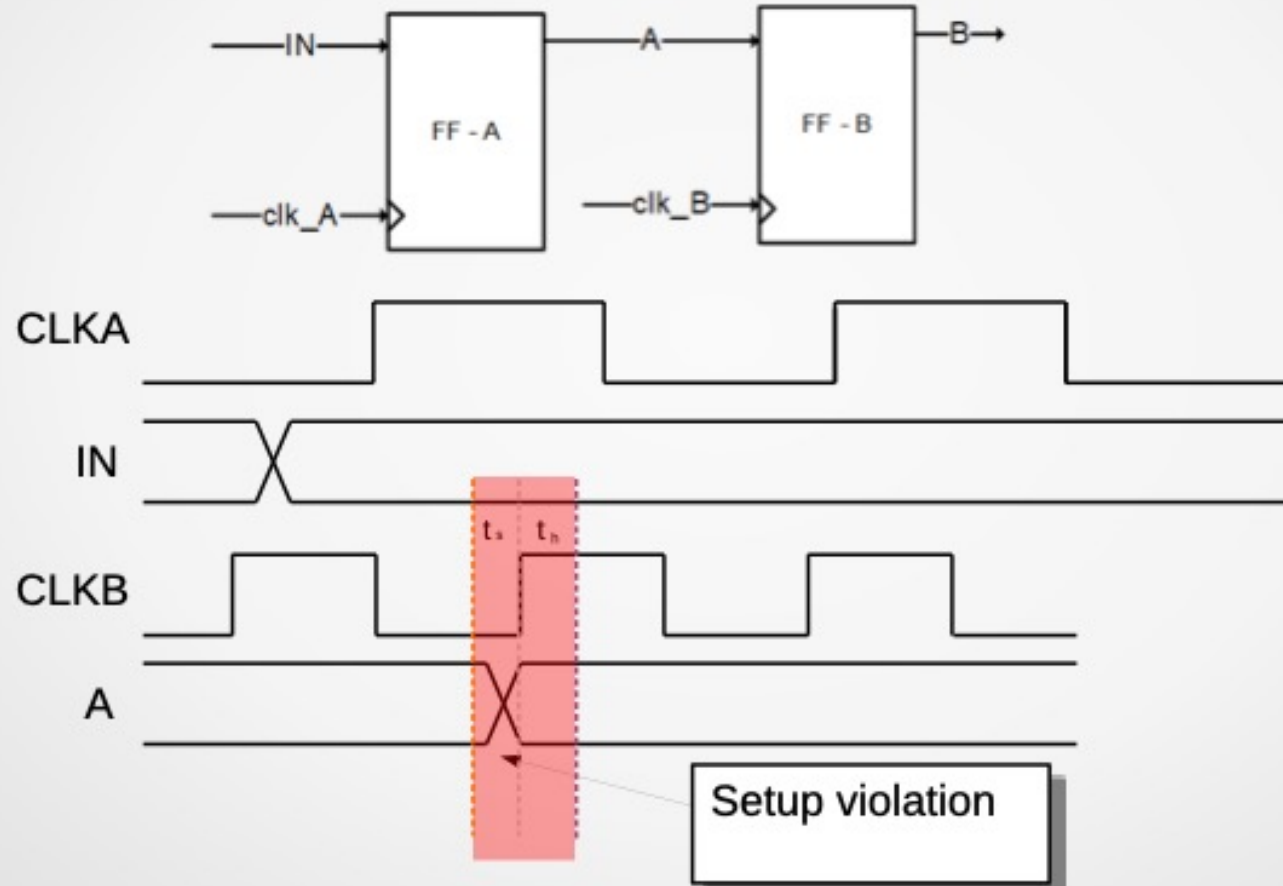


Because clk\_A and clk\_B are asynchronous, A can change anytime with regards to clk\_B rising edge.

## Who is responsible ?

- ▶ You are responsible for this. Designers must prevent **timing** problems:
  - External asynchronous signals must be handled properly with **synchronizers**,
  - when using multiple clock domains, use proper **clock domain crossing** (CDC) circuits,
  - look at **static timing analysis** report from your synthesis tool and take care (at least evaluate) of every (most) warnings.
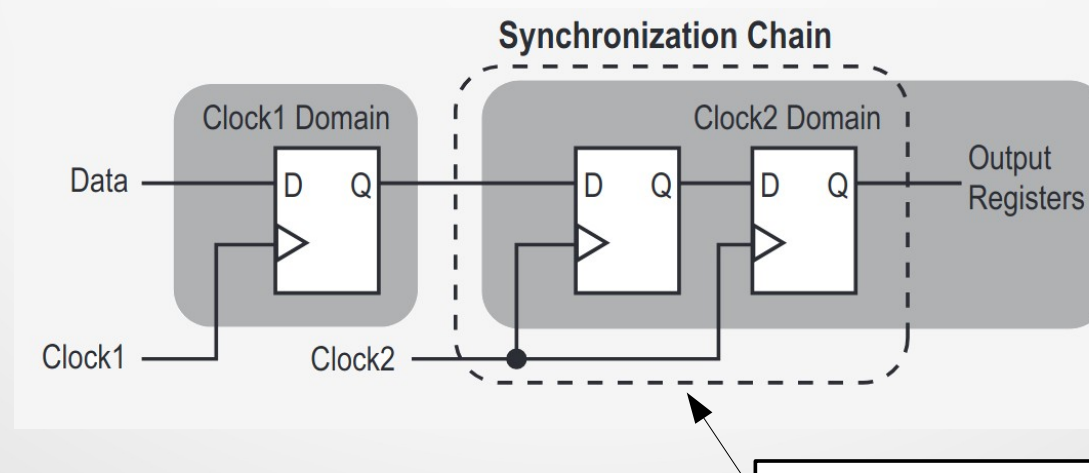
# Synchronizer

- ▶ Use a sequence of registers in the destination clock domain to resynchronize the signal to the new clock domain.
- ▶ Allows additional time for a potentially metastable signal to resolve to a known value before the signal is used in the rest of the design.



[https://trilobyte.com/pdf/golson\\_snug14.pdf](https://trilobyte.com/pdf/golson_snug14.pdf)

COLLSHADE - Introduction to digital design with Migen and Litex – v1.0

Must be kept close each other

[fjullien/migen\\_litex\\_tutorials \(github.com\)](https://github.com/fjullien/migen_litex_tutorials)



Under MIT license

# Clock Domain Crossing

- ▶ Used when transferring data (busses) across clock domain boundaries.
- ▶ Two methods:
  - Control based data synchronizers
  - FIFO based data synchronizers
 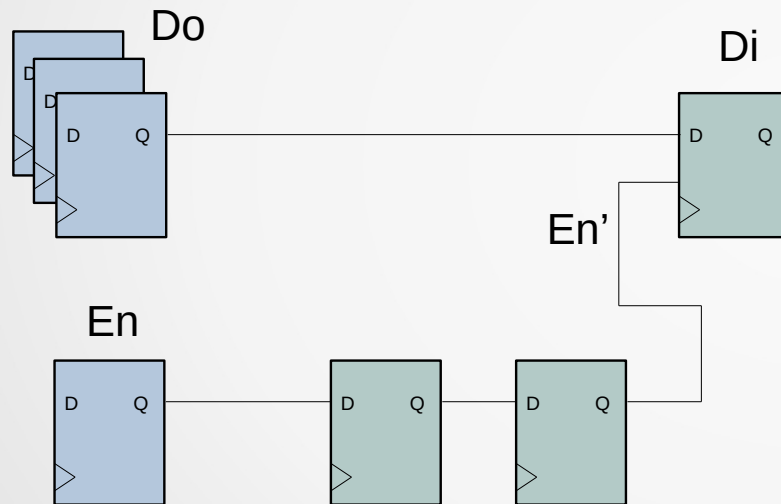
## Control based data synchronizers


- The enable signal is responsible to inform the receiving domain that data is stable and ready to be captured.



- Control based data synchronizer has limited bandwidth.
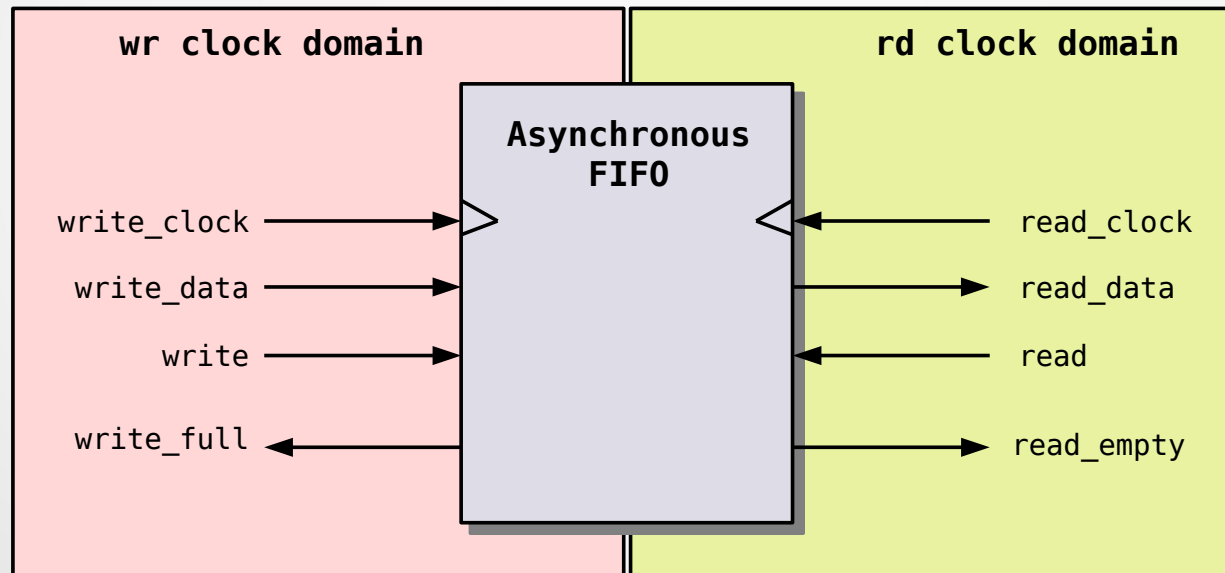
## FIFO based data synchronizers

- Data is pushed into the FIFO with transmitter clock and pulled out from FIFO with receiver clock.



## Static Timing Analysis

- ▶ Performed by the implementation tool
- ▶ Needs constraints (SDC files)
- ▶ Verify every path and detect potential failures at every corners
- ▶ Gives Fmax

Maximum possible analyzed clocks frequency

Clock Name	Period (ns)	Frequency (MHz)	Edge
pll0_clkout0	9.806	101.978	(R-R)

Geomean max period: 9.806

Launch Clock	Capture Clock	Constraint (ns)	Slack (ns)	Edge
pll0_clkout0	pll0_clkout0	10.000	0.194	(R-R)

# Static Timing Analysis

Maximum possible analyzed clocks frequency				
Clock Name	Period (ns)	Frequency (MHz)	Edge	
axi_clk	15.987	62.551	(R-R)	
mipi_pclk	7.077	141.293	(R-R)	
px_clk	12.711	78.671	(R-R)	

Geomean max period: 11.288

## Setup (Max) Clock Relationship

Launch Clock	Capture Clock	Constraint (ns)	Slack (ns)	Edge
axi_clk	axi_clk	12.500	-3.487	(R-R)
mipi_pclk	mipi_pclk	20.000	12.923	(R-R)
px_clk	px_clk	13.468	0.757	(R-R)

## Hold (Min) Clock Relationship

Launch Clock	Capture Clock	Constraint (ns)	Slack (ns)	Edge
axi_clk	axi_clk	0.000	0.086	(R-R)
mipi_pclk	mipi_pclk	0.000	0.184	(R-R)
px_clk	px_clk	0.000	0.307	(R-R)




# Outline


- Prevent metastability
- **Practice**
  - Implement PE, stacked PE
 
# Implement PE


- PE := Processing Element
  - Sequential FMA for  $V * V$  inner product
  - Reuse MAC of last week
- States
  - **INIT**
    - Wait for `in_init` signal
    - If `in_init` signal is non-0, reset MAC and next state is **EXEC**
    - NOTE `in_init` is of `cnt_bits`-bit
  - **EXEC**
    - Compute partial sum over `in_init` cycles
    - Then return to **INIT**



# Implement PE

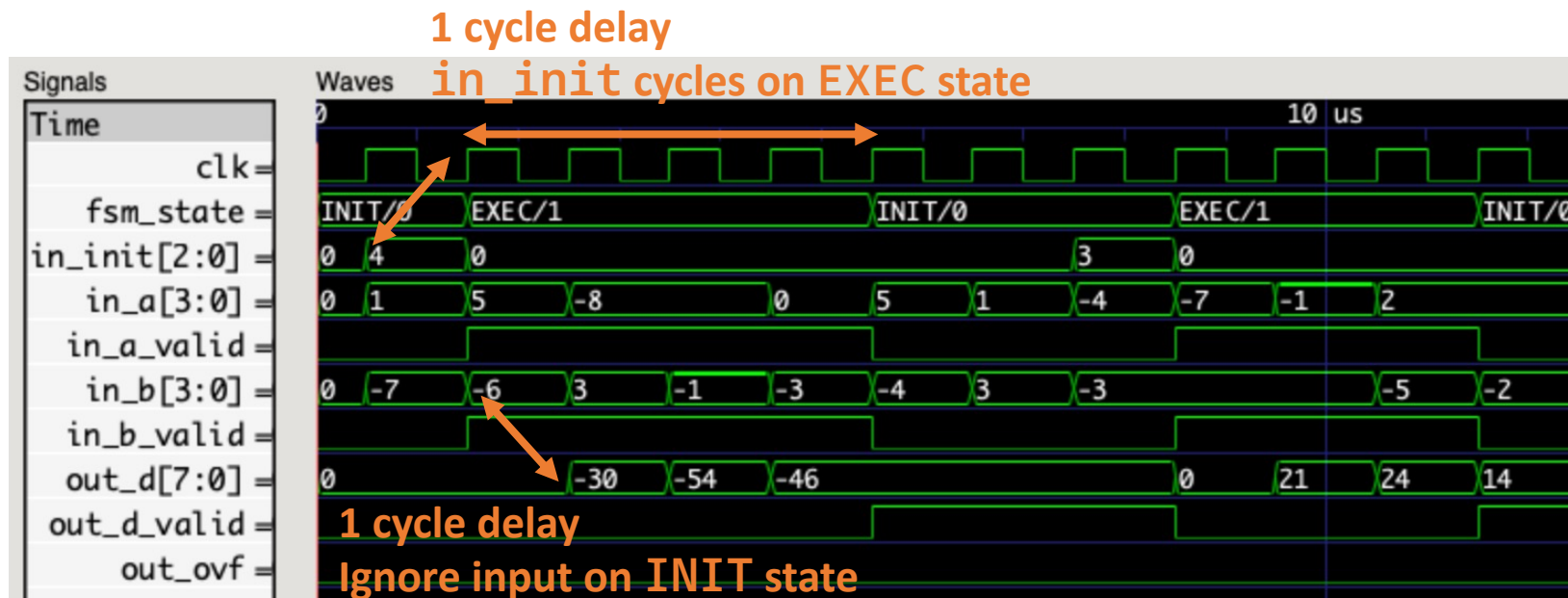


# Implement PE

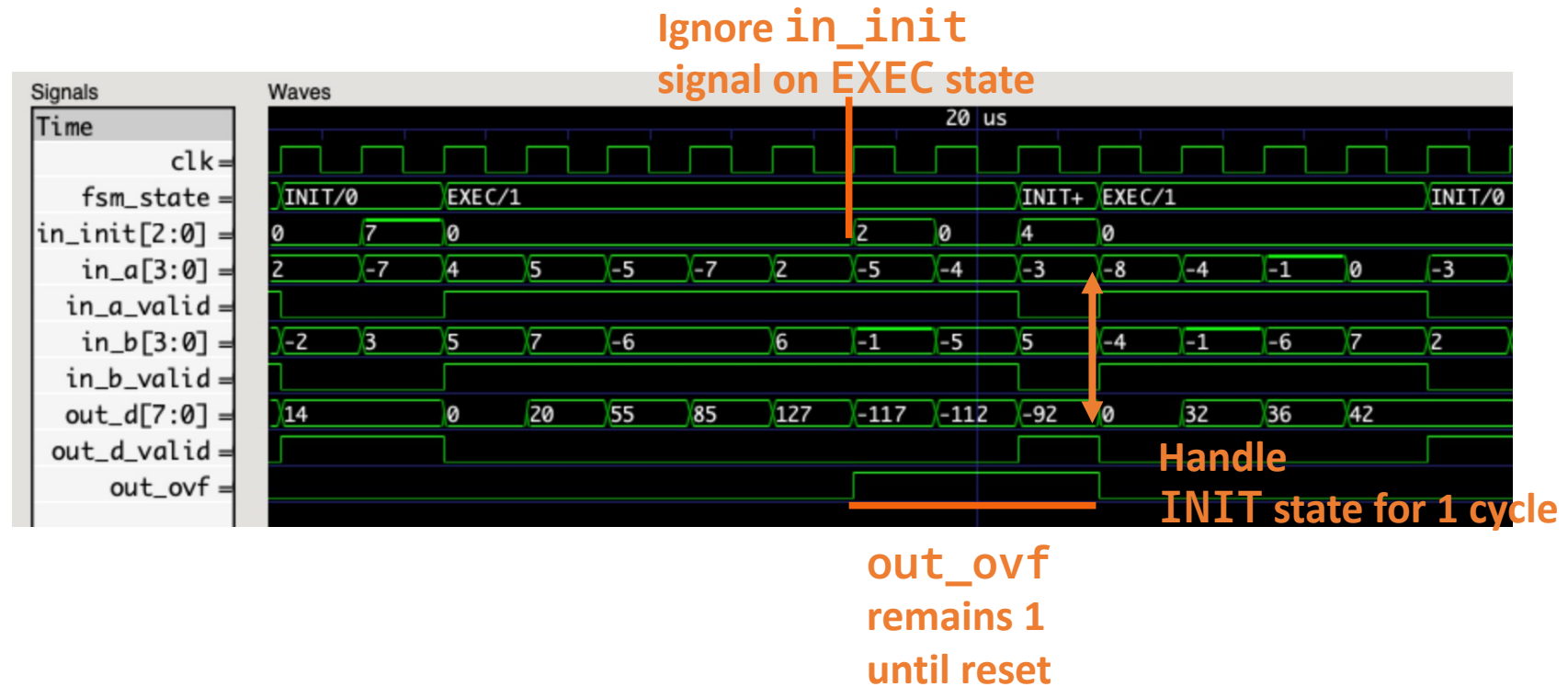

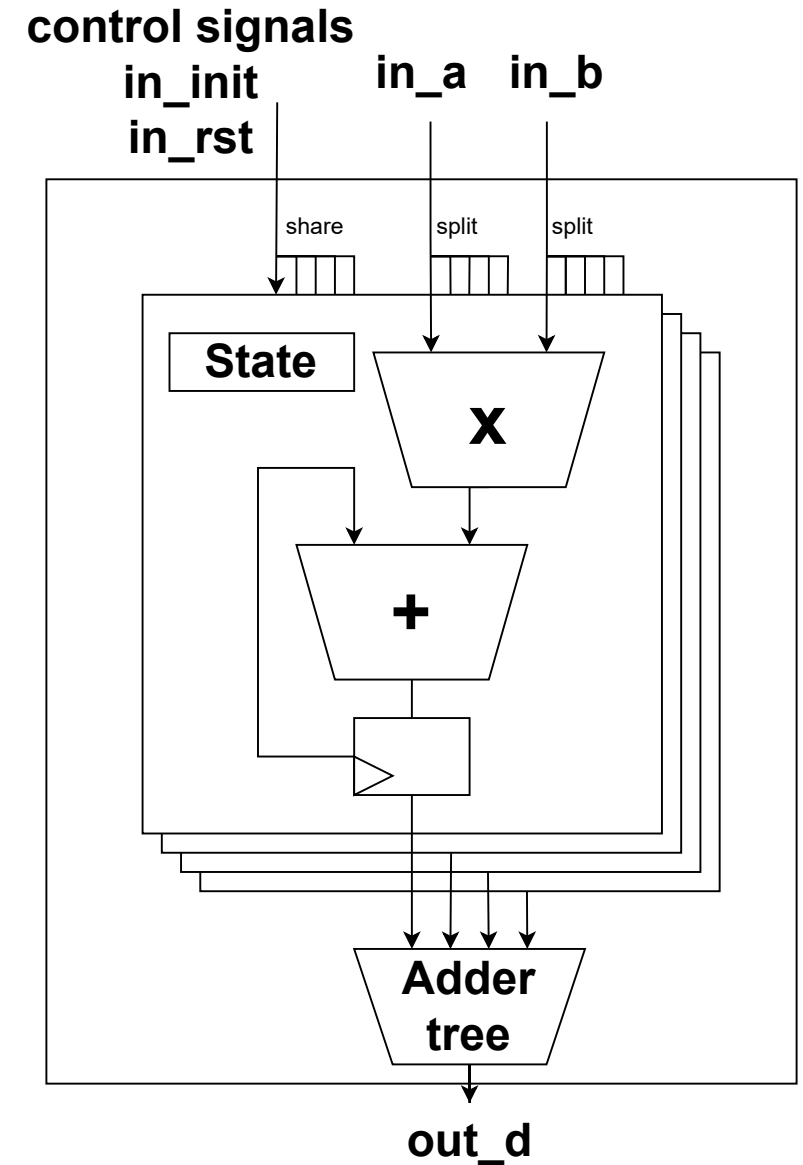
# Implement Stacked PE

- width-bit `in_a`, `in_b`
  - Split into multiple `num_bits` signals
- Reuse PE and AdderTree
  - Don't forget to add on `m.submodules`



# Implement Stacked PE

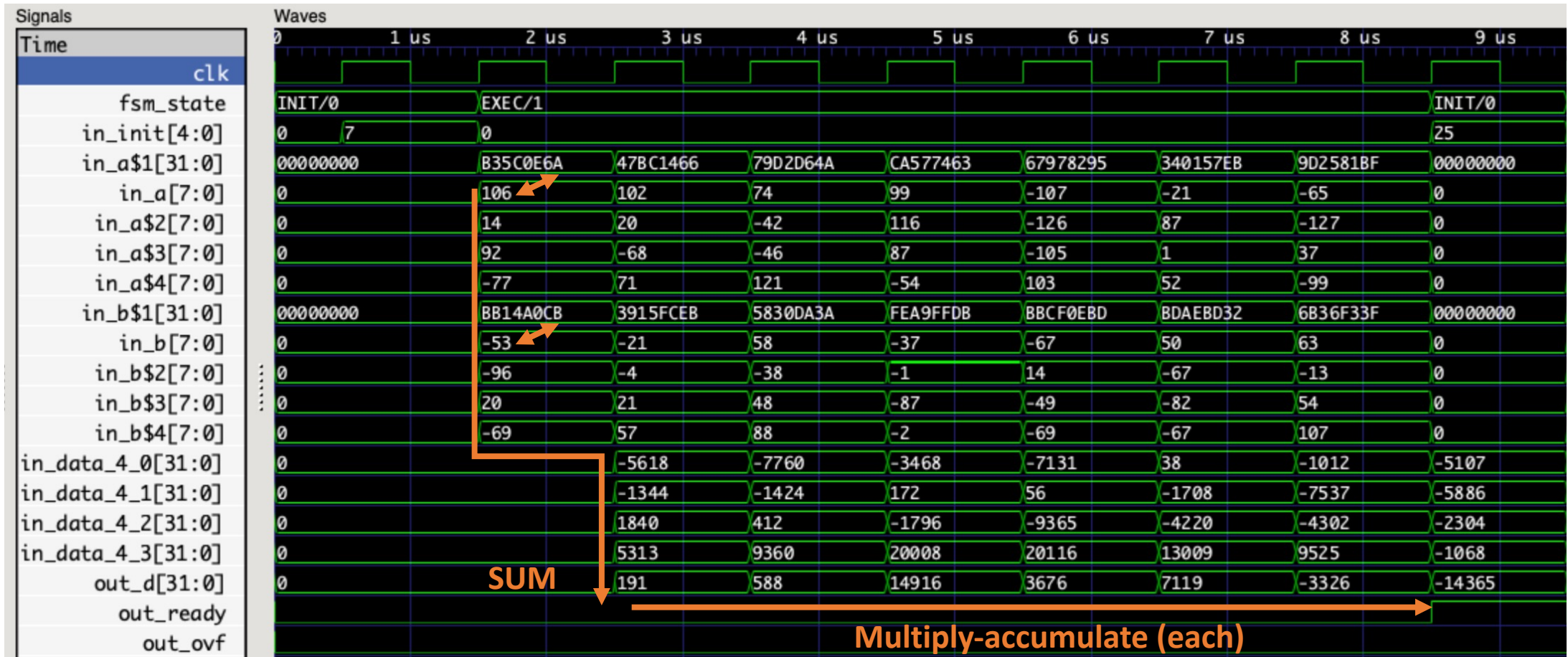

# Practice

- Skeleton code

<https://www.notion.so/skeleton-code-91e6f0b4d8b44ab1bccb71ee4f497cf2?pvs=4>

- Implement and show
  - Waveform
  - Code